

Section C

① Digital Electronics — 20 Q

② Computer Arch. — 15 Q

③ Microprocessor — 15 Q

Digital Electronics

≈ 40 Q / Marks.
≈

Trainer: Sohail Inamdar



1's and 2's Complement

- **1's Complement**

- The 1's complement of a number is found by changing all 1's to 0's and all 0's to 1's. This is called as 1's complement.

1 \rightarrow 0

0 \rightarrow 1

101011100
↓
010100011

- **2's Complement**

- The 2's complement of binary number is obtained by adding 1 to the Least Significant Bit (LSB) of 1's complement of the number.
- 2's complement = 1's complement + 1

101011100
← ←
010100100



WEIGHTED AND NON-WEIGHTED CODES

- **Weighted codes**

- Weighted binary codes are those binary codes which obey the positional weight principle. Each position of the number represents a specific weight.
- Examples of weighted code is BCD. In these codes each decimal digit is represented by a group of four bits.

- **Non-Weighted codes**

- In this type of binary codes, the positional weights are not assigned. The examples of non-weighted codes are Excess-3 code and Gray code.



BCD Number

$10 \rightarrow \underline{1010}, 6 = \underline{0110}$

- BCD – Binary Coded Decimal.
- In this code each decimal digit is represented by a 4-bit binary number.
- BCD is a weighted code its weight are 8421. BCD code are used only till 9 (0000 to 1001).
- ✓ BCD to Decimal.


$(\underline{0101} \ \underline{1000}) \text{ BCD} = (?)_{10} \underline{(58)}$ $(\underline{1001} \ \underline{0110}) \text{ BCD} = (?)_{10} \underline{(96)}$ $(\underline{0110} \ \underline{1000}) \text{ BCD} = (?)_{10} \underline{(68)}$ $(\underline{1000} \ \underline{0010}) \text{ BCD} = (?)_{10} \underline{(82)}$ $\boxed{0101 \ 1000} =$

✓ Decimal to BCD

$(\underline{6}) = (?) \text{ BCD} \rightarrow (\underline{0110}) \text{ BCD}$ $(254)_{10} = (?) \text{ BCD} \rightarrow (\underline{0010} \ \underline{0101} \ \underline{0100}) \text{ BCD}$
 $(168)_{10} = (?) \text{ BCD} \rightarrow (\underline{0001} \ \underline{0110} \ \underline{1000}) \text{ BCD}$ $(85) = (?) \text{ BCD}$

✓ Binary to BCD and BCD to Binary Conversion.

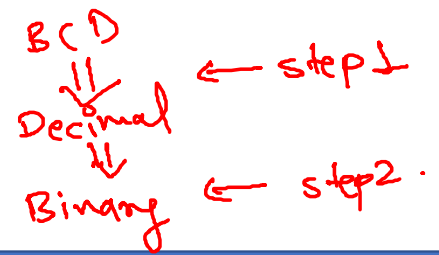- ✓ Step 1- Convert the binary/BCD number to decimal.
- ✓ Step 2- Convert decimal number to binary/BCD.



Excess-3 code

- The Excess-3 code is also called as XS-3 code.
- It is non-weighted code used to express decimal numbers.
- The Excess-3 code words are derived from the 8421 BCD code words by adding (0011) (3) to each code word in 8421.

① Decimal to Excess-3

- ✓ Step 1- Convert decimal to BCD.
- ✓ Step 2- Add 3 (0011) to this BCD number.

$$\begin{array}{lcl} (5)_{10} & \Rightarrow & 0101 \Rightarrow \\ \text{Decimal} & & \text{BCD} \end{array} \Rightarrow 0101 + 0011 = \boxed{1000} \text{ Excess-3}$$

② Excess-3 to Decimal

- ✓ Step 1- Subtract (0011)₂ from each 4 bit of excess-3 digit to obtain the corresponding BCD code.
- ✓ Step 2- Convert BCD to Decimal.

$$1000 \rightarrow \text{Excess 3}$$

$$\text{step 1} \rightarrow \underline{0011}$$

$$0101 \rightarrow \text{BCD}$$

$$5 \rightarrow \text{Decimal}$$

③ Binary to Excess-3

- ✓ Step 1- Convert Binary to decimal.
- ✓ Step 2- Convert decimal to BCD.
- ✓ Step 3 - Add 3 (0011) to this BCD number.



Gray Code

- It is the non-weighted code and it is not arithmetic codes.
- There are no specific weights assigned to the bit position.
- It has a very special feature that, only one bit will change each time the decimal number is incremented (only one bit changes at a time).
- Gray code is popularly used in the shaft position encoders.

4 3 2 1 0
2 2 2 2 2
1 0 0 0 1

Decimal Number		Gray Code
0	→	0000
1	→	0001
2	→	0011
3	→	0010
4	→	0110
5	→	0111
6	→	0101

- ① It changes by 1 bit at a time
② On each iteration pattern will not be repeated.

0000 → 0
0001 → 1
0011 → 2 -
0010 → 3 -
0110 → 4 -
0111 → 5 -
0101 → 6 -
0100 → 7 -
1100 → 8



Boolean algebra

- Algebra that deals with binary number system
- George Boole developed it for simplification and manipulation of logic
- Boolean algebra uses
 - ✓ + Binary digits - 0 and 1
 - + Logical addition '+' also known as 'OR' which follows law of binary addition
 - + Logical Multiplication '.' also known as 'AND' which follows law of binary multiplication
 - + Complementation '-' also known as 'NOT' which follows law of binary complement
- ✓ Boolean algebra is used to simplify Boolean expressions which represent combinational logic circuits.
- ✓ **Operator precedence (scanned from left to right)**
 - ✓ ()
 - ✓ NOT
 - ✓ AND
 - ✓ OR



Boolean Function

- Boolean function is expression formed with
 - ✓ + Binary variables
 - ✓ + Operators (AND, OR, NOT)
 - + Parentheses and equal to sign
- Value of Boolean function can be either 0 or 1
- Boolean function can be represented as an algebraic expression or a truth table
e.g. $W = f(x, y, z)$
Where, W is a function
x, y, z are variables or literals

✓ • Minimization of Boolean functions

Minimization deals with

- + Reduction in number of variables
- + Reduction in number of terms

- There are 2 methods to minimize any Boolean function
 - ✓ + Using Boolean laws
 - ✓ + Using K-map



Laws of Boolean Algebra

✓ Idempotent Law

- $A * A = A$ $1 * 1 = 1$
- $A + A = A$ $1 + 1 = 1$

✓ Associative Law

- $(A * B) * C = A * (B * C)$
 - $(A + B) + C = A + (B + C)$
- Commutative Law**
- $A * B = B * A$
- $A + B = B + A$
- Handwritten example for the commutative law of addition:
- $$\begin{array}{l|l} (1+0)+1 & 1+(0+1) \\ \hline = 1+1 & = 1+1 \\ = 1 & = 1 \quad \checkmark \end{array}$$

- Commutative Law

- ✓ $A * B = B * A$
✓ $A + B = B + A$

• Distributive Law

- $A * (B + C)$ = $A * B$ + $A * C$
- $A + (B * C)$ = $(A + B)$ * $(A + C)$

✓ Identity Law

- $A * 0 = 0$ $A * 1 = A$
- $A + 1 = 1$ $A + 0 = A$

Complement Law

- $A * \sim A = 0$ $1 * (\sim 1) = 1 * 0 = 0$
- $A + \sim A = 1$ $1 + (\sim 1) = 1 + 0 = 1$

• Involution Law

- $\sim(\sim A) = A$

✓ DeMorgan's Law

- $\sim(A * B) = \sim A + \sim B$
- $\sim(A + B) = \sim A * \sim B$



Standard Form

$$A = 1 \rightarrow A$$
$$A = 0 \rightarrow \overline{A}$$

✓ Minterm

- + Minterm is a product or AND term
 - + contains n variables with 2^n possible combinations
 - + variables either in normal or in complemented form
- e.g. ABC , $A'BC$, $AB'C'$

$$A \star B \star C$$

$$\overline{A} \overline{B} \overline{C}$$

✓ Maxterm

- + Maxterm is a sum or OR term
 - + contains n variables with 2^n possible combinations
 - + variables either in normal or in complemented form
- e.g. $A+B+C$, $A+B'+C$

$$\overline{A} + B + \overline{C}$$

✓ Sum of product (SOP) expression

SOP expression is minterm or minterms logically added (ORed) together.

e.g. $A'B + AB$

$$\underline{A \times B} + \underline{B \times C}$$

✓ Product of sum (POS) expression

POS expression is maxterm or maxterms logically multiplied (ANDed) together.

e.g. $(A+B) \cdot (A'+B)$

$$\underline{A + B} \star \underline{A + C}$$



Standard Form

$$\begin{array}{l} A = 1 \\ \bar{A} = 0 \end{array}$$

sum of products.

- Solve the $X(A,B,C) = A + BC$ convert in Standard SOP form

$$\begin{aligned} \Rightarrow A &= A(B + \bar{B}) \\ &= AB + A\bar{B} \\ &= AB(C + \bar{C}) + A\bar{B}(C + \bar{C}) \\ &\Rightarrow ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} \end{aligned}$$

$$\begin{aligned} BC &= BC(A + \bar{A}) \\ &= BCA + BC\bar{A} \\ &\rightarrow = ABC + \bar{A}BC \end{aligned}$$

$$\begin{aligned} \underline{A + BC} &= \underline{ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC + \bar{A}BC} \\ &= \underline{ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC} \\ &\quad \begin{array}{ccccc} \underline{111} & \underline{110} & \underline{101} & \underline{100} & \underline{011} \\ = & 7 & 6 & 5 & 4 & 3 \end{array} \end{aligned}$$

$$\Sigma(7, 6, 5, 4, 3)$$

$$X(A,B,C) = \underline{\Sigma(3, 4, 5, 6, 7)}$$



K-Map

- Karnaugh introduced a simplification of Boolean functions in an easy way.
- This method is known as Karnaugh map method or K-map method.
- It is a pictorial representation of graphical method, which consists of 2[#] cells for 'n' variables. The adjacent cells are differed only in single bit position.
- K-map uses Gray code.

- 2- bits

A \ B	0	1
0	0 th	1 st
1	2 nd	3 rd

- 3-bits

A \ BC	<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
0	0 th	1 st	3 rd	2 nd
1	4 th	5 th	7 th	6 th



K-Map

• Karnaugh Map Simplification Rules-

- To minimize the given Boolean function, we draw a K-Map according to the number of variables it contains.
- We fill the K-Map with 0's and 1's according to its function. Then, we minimize the function in accordance with the following rules.
- **Rule-1:**
 - We can either group 0's with 0's or 1's with 1's but we can not group 0's and 1's together.
 - X representing don't care can be grouped with 0's as well as 1's.
- **Rule-02:**
 - Groups may overlap each other.
- **Rule-03:**
 - We can only create a group whose number of cells can be represented in the power of 2.
 - In other words, a group can only contain 2^n i.e. 1, 2, 4, 8, 16 and so on number of cells.



K-Map

- **Rule-4:**

- Groups can be only either horizontal or vertical.
- We can not create groups of diagonal or any other shape.

- **Rule-5:**

- Each group should be as large as possible.

- **Rule-6:**

- Opposite grouping and corner grouping are allowed.

- **Rule-7:**

- There should be as few groups as possible.



K-Map

- Simplify the Boolean function $F(A,B,C) = \Sigma(1,5,6,7)$
 - Simplify the Boolean function $F(A,B,C) = \Sigma(0,1,3,4,5)$
 - Simplify the Boolean function $F(A,B,C,D) = \Sigma(0,2,4,6,8,9,10)$
- } H.W.

$$F(A,B,C) = \Sigma(1,5,6,7)$$

$$2^n = 2^3 = 8$$

A \ BC	BC			
	00	01	11	10
0		1		
1		1	1	1

⇒

A \ BC	BC	
	01	11
0	1	
1	1	

$\overline{B}C$

A \ BC	BC	
	11	10
1	1	1

$A \cdot B$

$$AB + \overline{B}C$$



Logic Gates

What are logic gates :-

- It is physical device which performs logical operation on one or more logical i/p(s) and produces a single logical o/p.
- Logical operations :- inversion, logical multiplication, logical sum etc.

Categories:-

- I. Basic Gates : AND, OR, NOT.
- II. Universal Gates : NAND, NOR
- III. Arithmetic Gates : X-OR, X-NOR



Logic Gates

Truth Table


- A truth table shows how a logic circuit responds to various combinations of i/p, using logic 1 for true and 0 for false.
- Formula for truth table :-** $2^n = m$
- Where,
 - $n \rightarrow$ number of inputs
 - $M \rightarrow$ combination of inputs

$$2^n = m$$

$$2^1 = 2$$

$$2^2 = 4$$

➤ NOT Gate :-

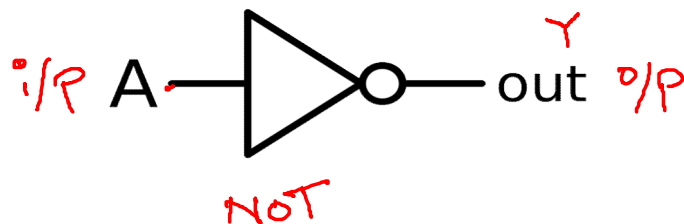


A	Y
0	1
1	0




Logic Gates

AND Gate:

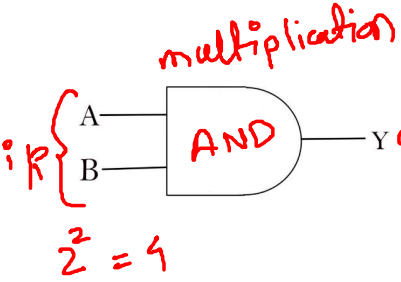


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate:

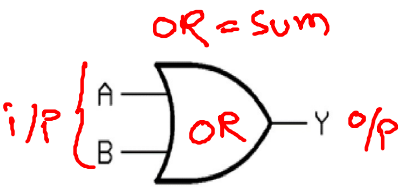


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NAND Gate:

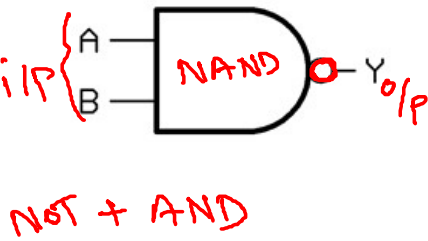

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate:

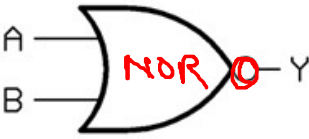


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0




Logic Gates

• XOR Gate :-

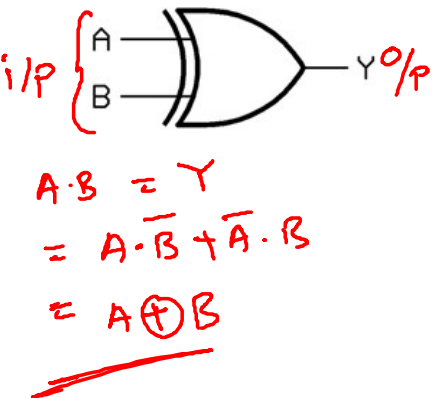

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Gate :-

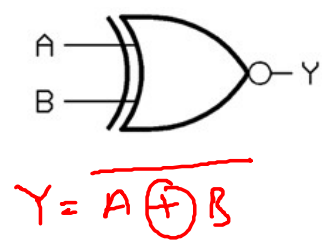

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

• Ques.

XNOR Gate, with 5 i/p.

i.e. 101010 → 0 O/p ?



Universal Gate

- A Universal gate is a logic gate which can implement any Boolean function without the need to use any other type of logic gate.
- NAND gate and NOR gate are universal gate.
- Any logic circuit can be built using NAND gate or NOR gate.




Combinational Circuits & Sequential Circuit

Digital Electronics

Combinational Circuits

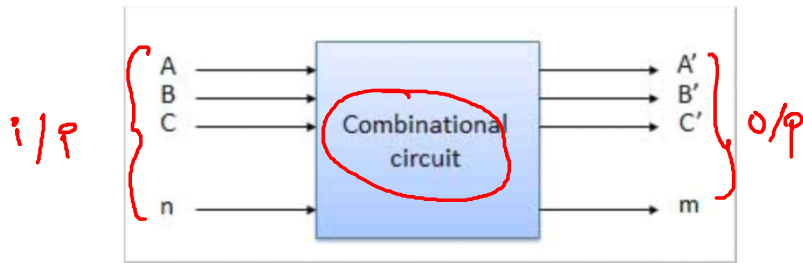
- O/p is only depending on the present I/p.



- No feedback. ✗
- No memory. ✗

Sequential Circuit

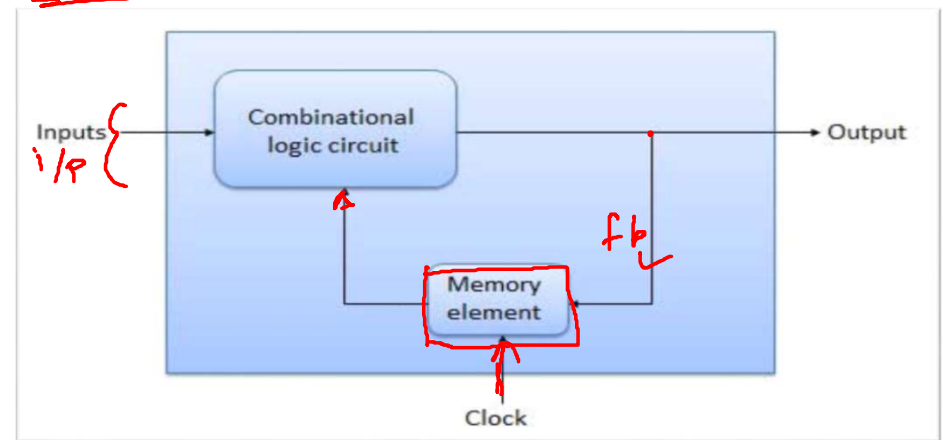- O/p is depending on the present I/p as well as past outputs.



Combinational Circuits & Sequential Circuit


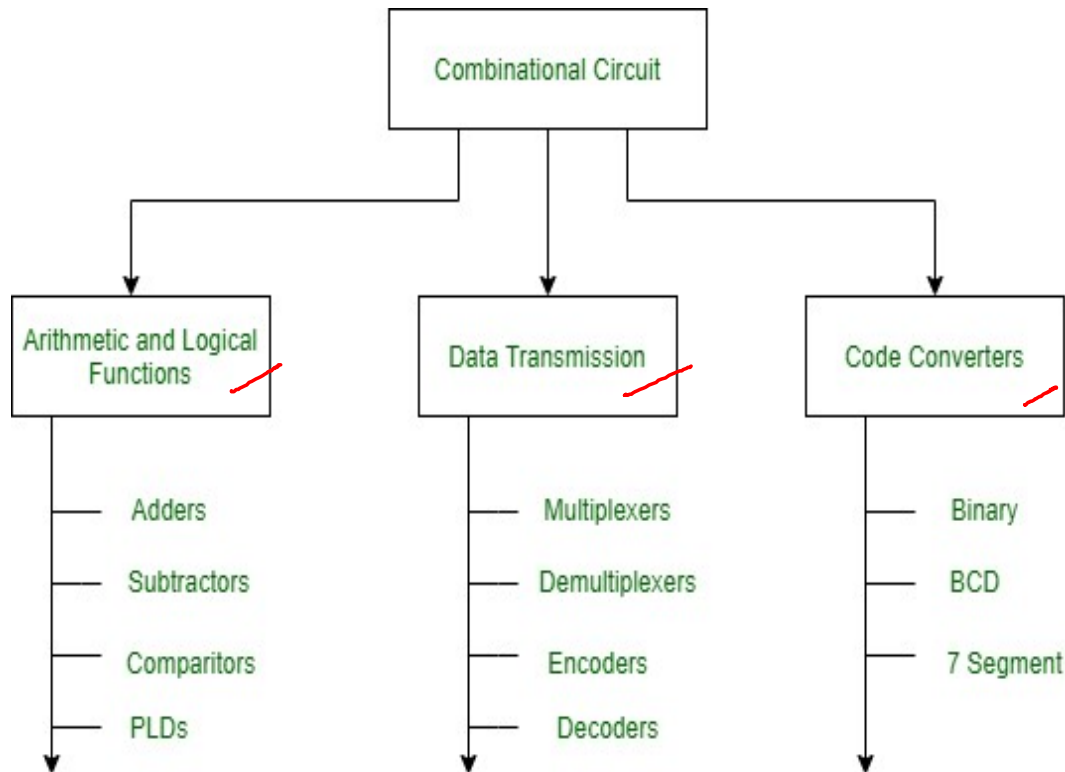


Figure - Classifications of Combinations Circuits

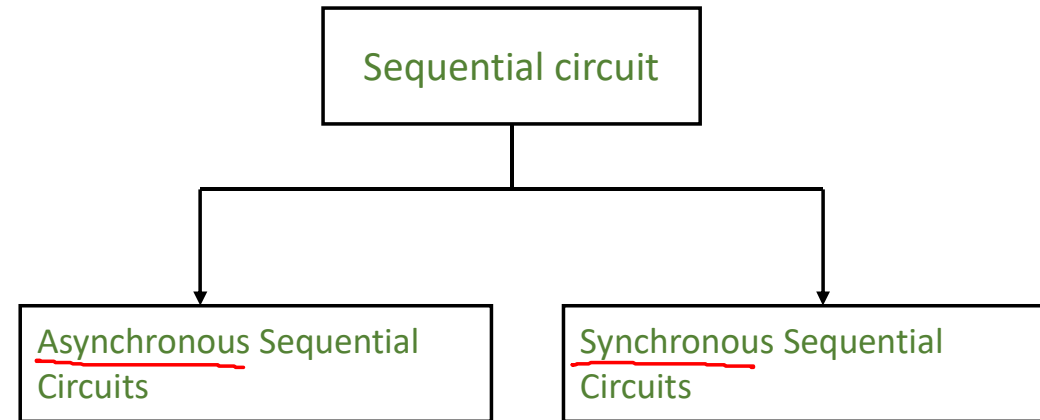


Combinational Circuits

- ✓ **Combinational Logic Circuits** are made up from basic logic AND, OR, NAND, NOR, or NOT gates that are “combined” or connected together to produce more complicated switching circuits.

- Combinational circuits consist

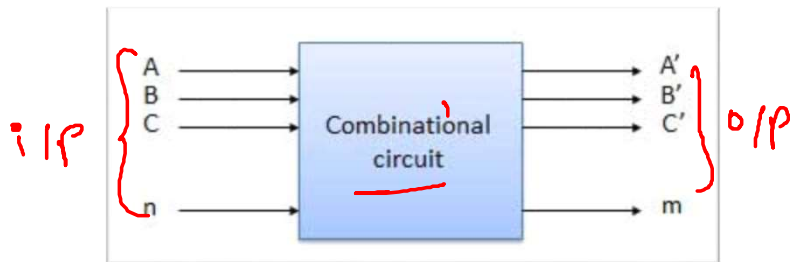- ✓ Input variables
- ✓ Logic Gates
- ✓ Output variables



$$Y = F(X)$$

Where,

$$X = \{x_0, x_1, x_2, \dots, x_{n-1}\}$$

$$Y = \{y_0, y_1, y_2, \dots, y_{n-1}\}$$

- ✓ **Design Procedure**

- ✓ 1. Define the problem statement
- ✓ 2. Determine number of input and output variables
- ✓ 3. Assign letter symbols ✓
- ✓ 4. Construct a truth table
- ✓ 5. Obtain simplified Boolean Expression
- ✓ 6. Draw a logic diagram



Designing of Combinational Circuit

Step 1: Problem statement

Design a circuit with 3 inputs which produce a logic 1 output when more than one inputs are logic 1.

Step 2: Input – 3 Output – 1


Step 3: Input variables – A, B, C Output variable – Y

Step 4: Truth Table

$2^3 = 8$


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Step 5 : Simplified Boolean Expression

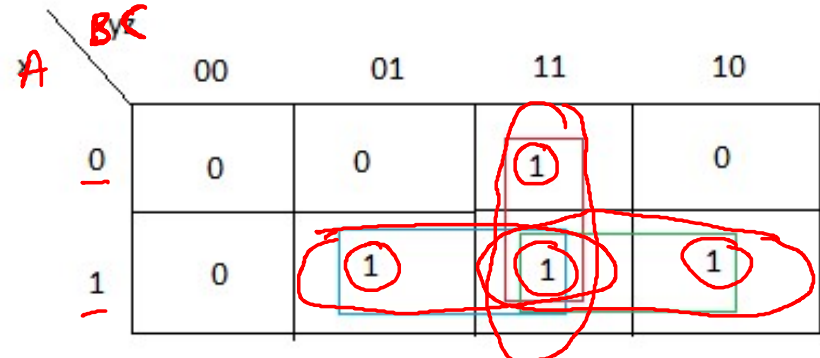


$Y = AC + BC + AB$

Step 6: Logic Diagram

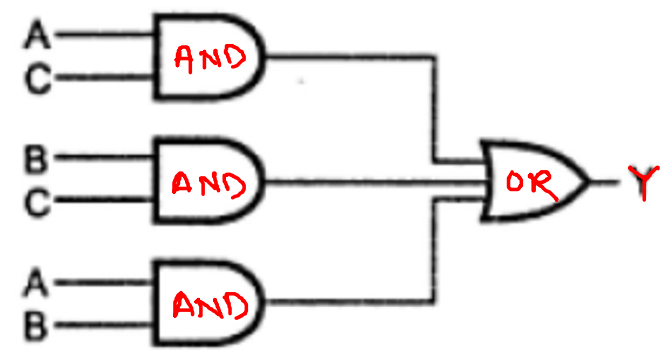

Half Adder

- Used to add two single bit numbers

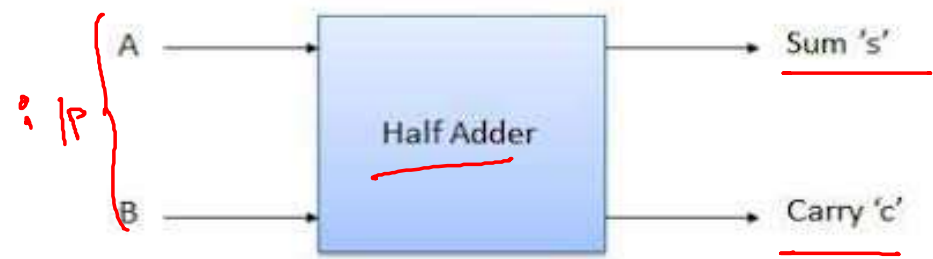

Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean Expressions

For Carry

A \ B	0	1
0	0	0
1	0	1

Carry = AB

For Sum

A \ B	0	1
0	0	1
1	1	0


$A\bar{B} + \bar{A}B$

Sum = $A\bar{B} + \bar{A}B$
 $= A \oplus B$

$C = A.B$


$S = A \oplus B$

Logic Diagram

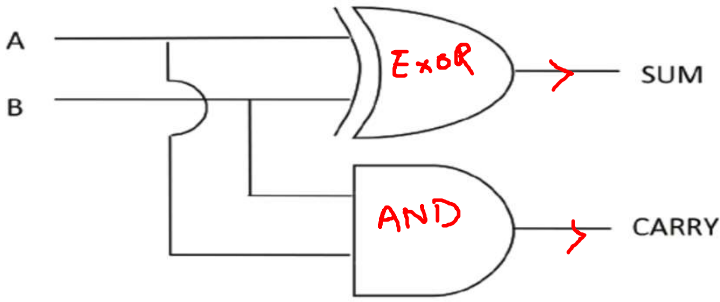

Full Adder

- Used to add 1 bit numbers with carry

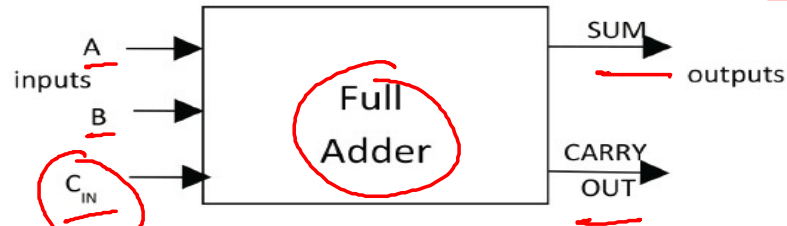

Truth Table

A	B	C_{an}	S	C_{oot}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Expressions

For Carry (C_{out})

BC_{in}	00	01	11	10
A	0	0	1	0
1	0	1	1	1

$$C_{out} = AB + A C_{in} + B C_{in}$$


For Sum

BC_{in}	00	01	11	10
A	0	1	0	1
1	1	0	1	0

$$Sum = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$


$$S = A \oplus B \oplus C_i$$

Logic Diagram

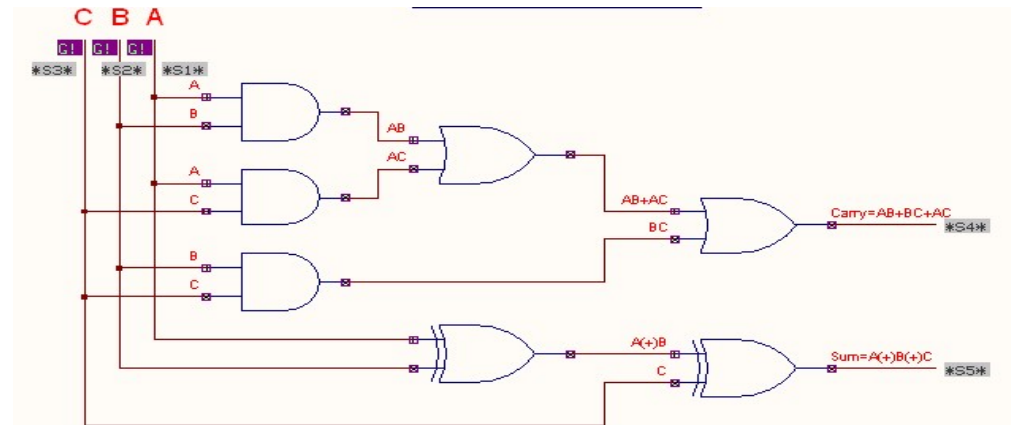

Half Subtractor

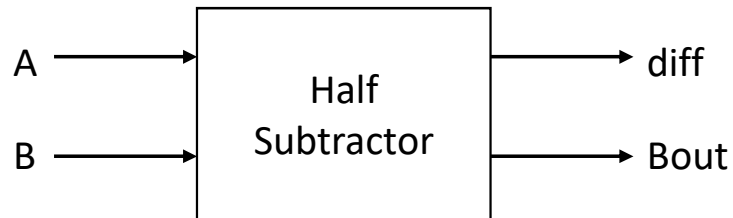- Used to subtract two single bit numbers



Truth Table

A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean Expressions

For Difference

A \ B	0	1
0	0	1
1	1	0


$$\begin{aligned}\text{Difference} &= A\bar{B} + \bar{A}B \\ &= A \oplus B\end{aligned}$$

For Borrow

A \ B	0	1
0	0	1
1	0	0


$$\text{Borrow} = \bar{A}B$$

Logic Diagram

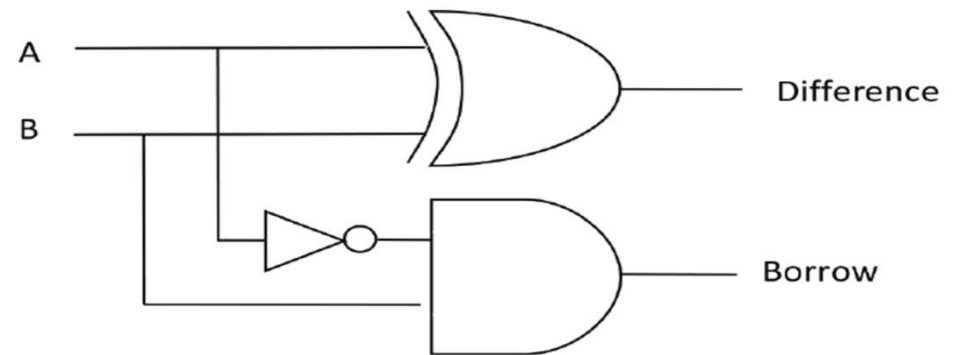

Full Subtractor

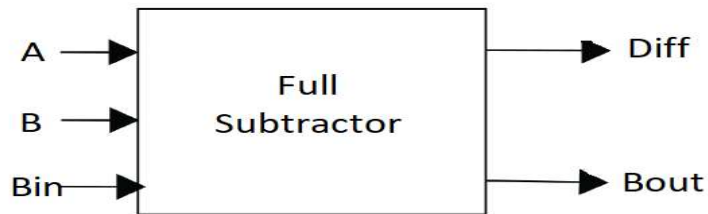- Used to subtract 1 bit numbers with borrow



Truth Table

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Boolean Expressions

For D

BB _{in}	00	01	11	10
A				
0	0	1	0	1
1	1	0	1	0


$$D = \bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + A\bar{B}B_{in} + AB\bar{B}_{in}$$

For B_{out}

BB _{in}	00	01	11	10
A				
0	0	1	1	1
1	0	0	1	0


$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$

Logic Diagram

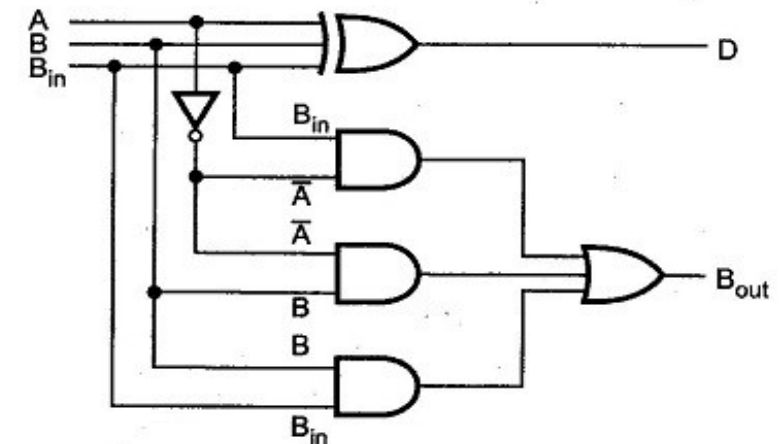


Multiplexers

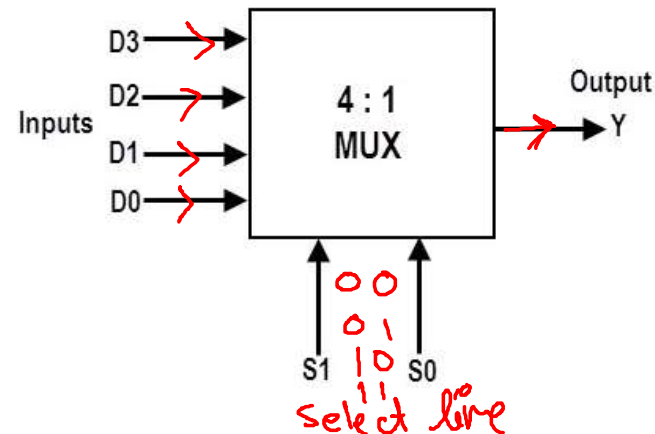- Multiplexer is a Combinational circuit that selects binary information from one of many input lines and directs it to o/p line.
- Selection of input line is controlled by group of select lines.
- Select lines = n
- No. of inputs = 2^n
- Types of MUX:-
 - 2-to-1 (1 select line)
 - 4-to-1 (2 select lines)
 - 8-to-1 (3 select lines)
 - 16-to-1 (4 select lines)




Multiplexers

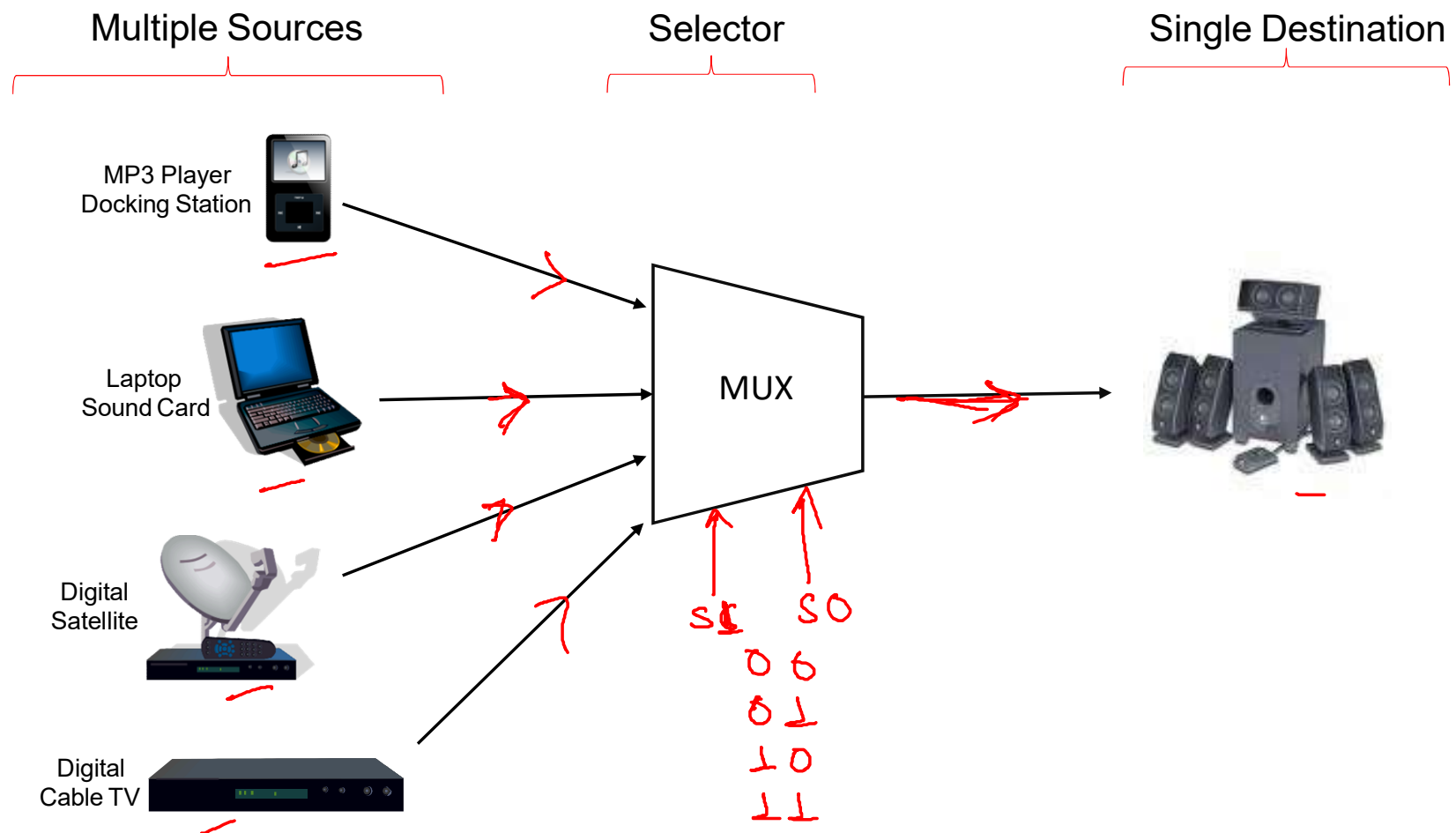

Multiplexers

- 2:1 MUX

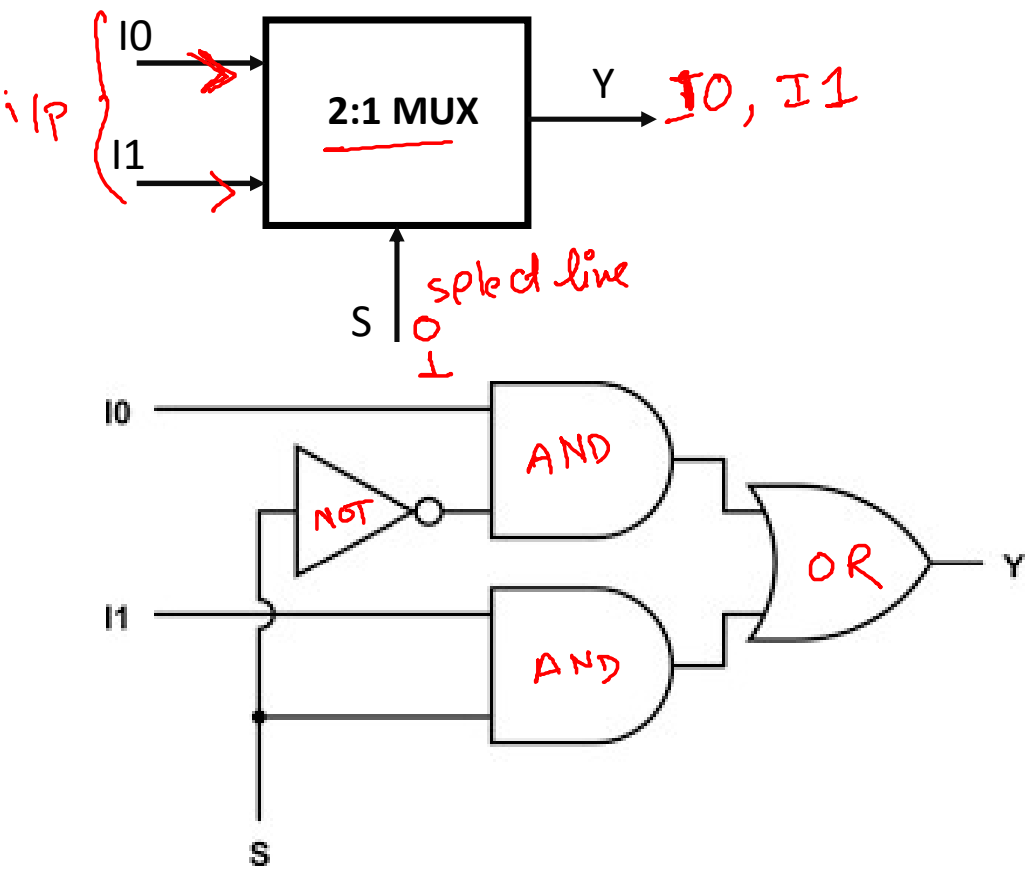

✓

<u>S</u>	<u>I0</u>	<u>I1</u>	<u>Y</u>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


✓

S	Y
<u>0</u>	<u>I0</u>
<u>1</u>	<u>I1</u>




Multiplexers

- 4-to-1 (2 select lines)

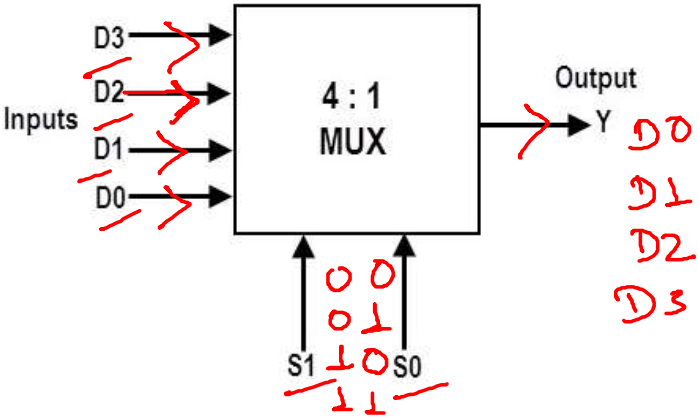


Select data inputs		Output
S1	S0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

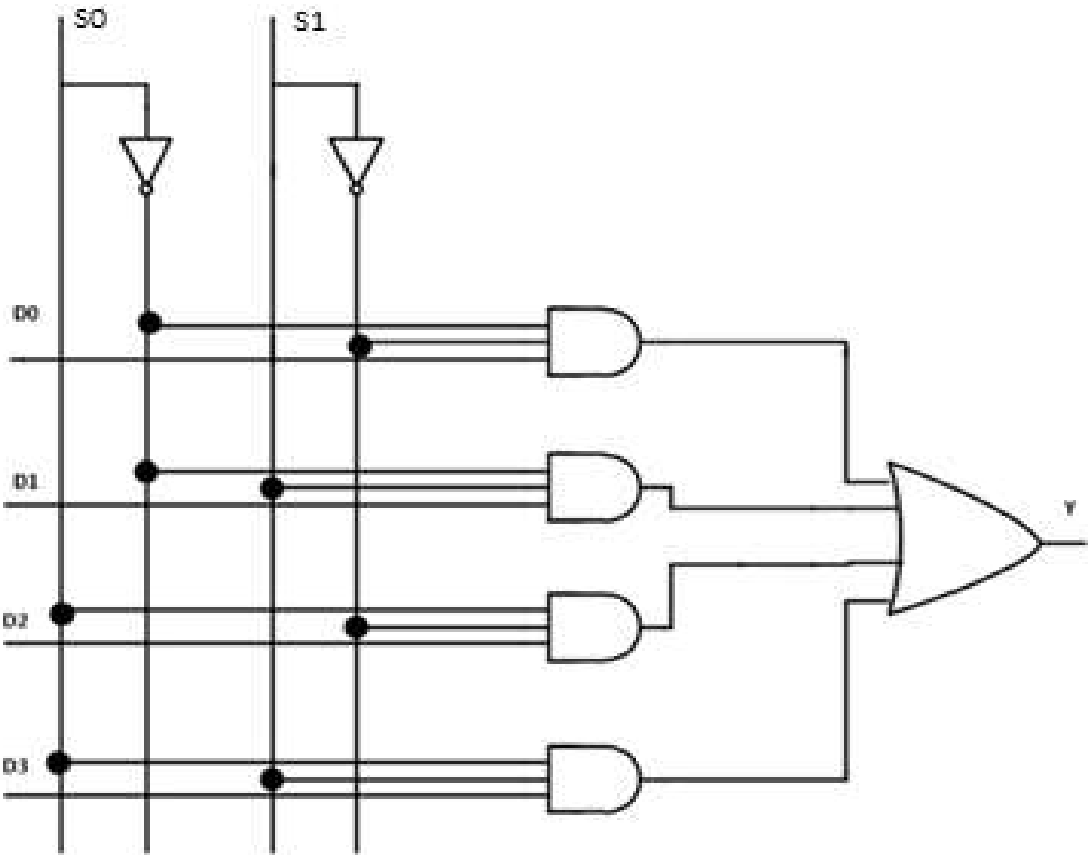


Demultiplexers

- A DEMUX is a digital switch with a single input (source) and a multiple outputs (destinations).
- Selection of output line is controlled by select lines.
- Select lines = n ,
- no. of outputs = 2^n
- Types of DEMUX:-

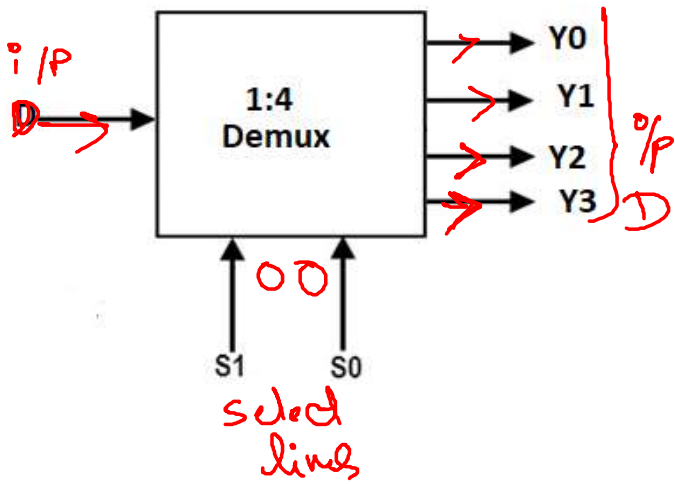- 1-to-2 (1 select line)
- 1-to-4 (2 select lines)
- 1-to-8 (3 select lines)
- 1-to-16 (4 select lines)



S1	S0	Y3	Y2	Y1	Y0
<u>0</u>	<u>0</u>	D	0	0	0
<u>0</u>	<u>1</u>	0	D	0	0
<u>1</u>	<u>0</u>	0	0	D	0
<u>1</u>	<u>1</u>	0	0	0	D

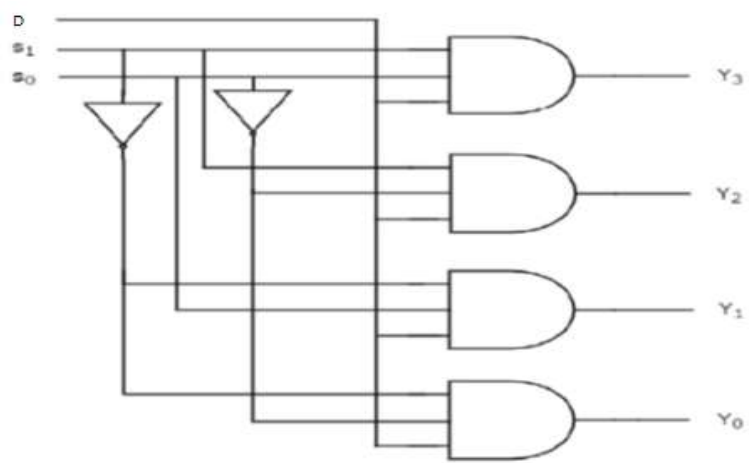

Demultiplexers

